


ASSIGNMENT -1

GROUP 3

Kshitij Agrawal
(17EC10063)


Aadi Swadipato Mondal
(17EC10065)

CIRCUIT DIAGRAM

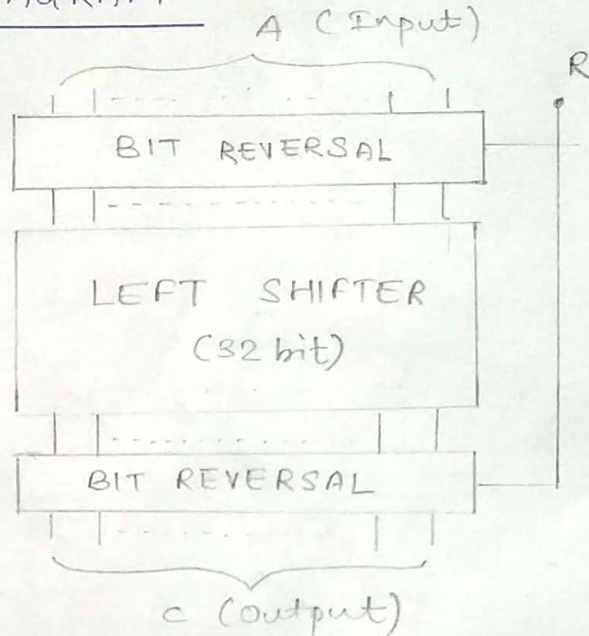

Structure of Left Right Shifter

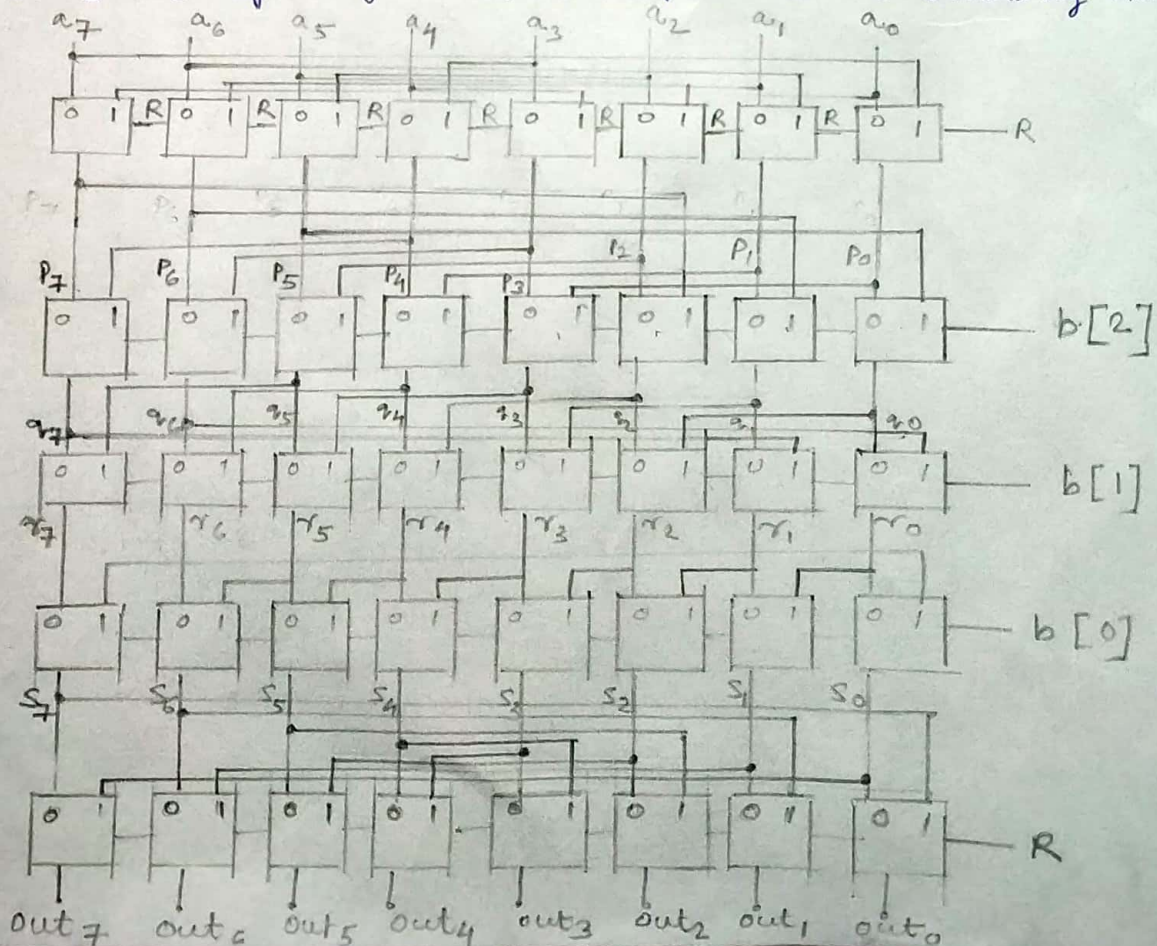* For 8-bit left Right barrel shifter. Can be similarly extended to 32 bit




The total num. of 2×1 mux used is

$$(5 + 2) \times 32 = 7 \times 32 \text{ MUX}$$

\uparrow for shifting \uparrow for bit reversal

Answer these questions

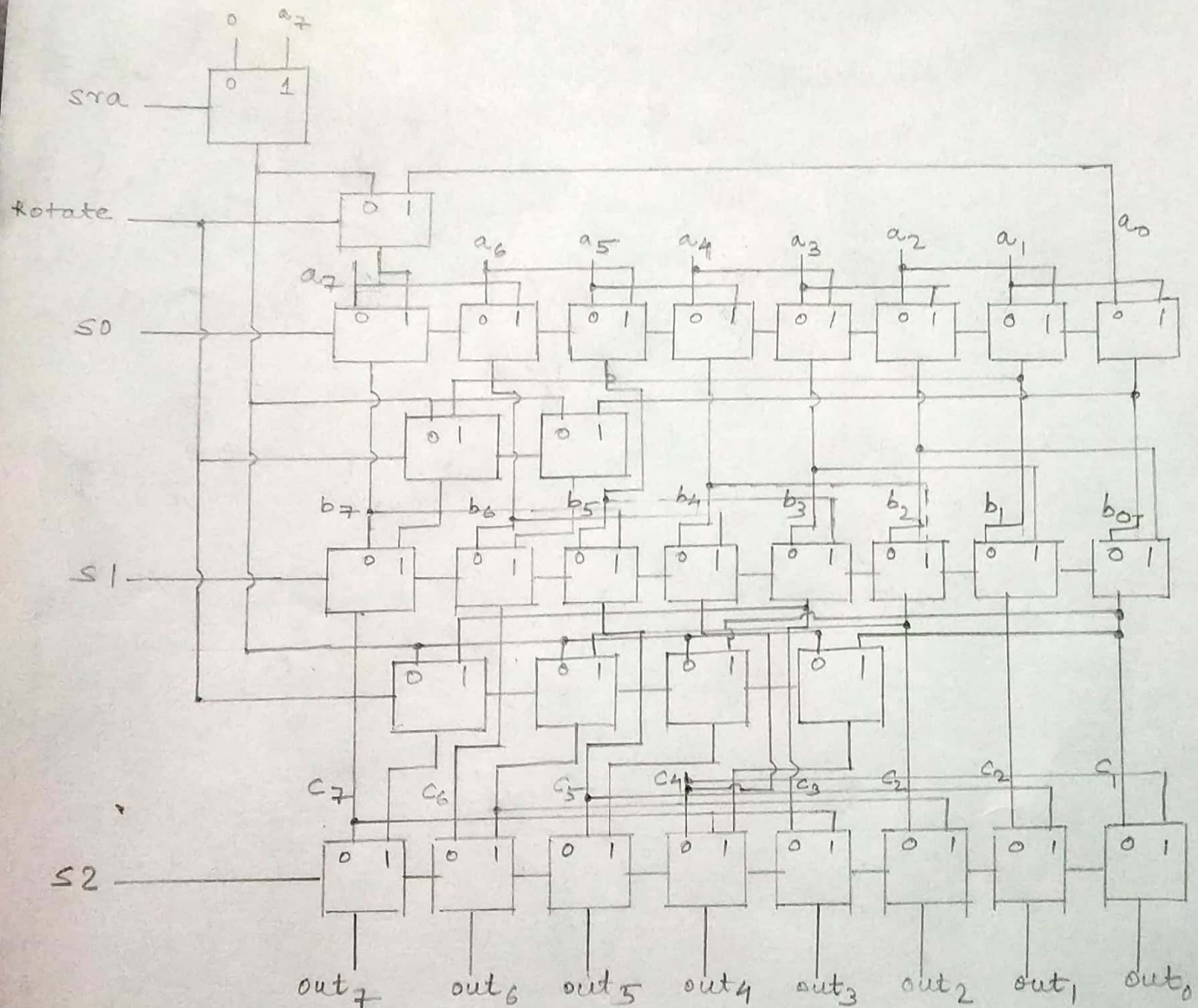

Working

we use $1 \text{ mux}(2 \times 1)$ to decide between shift logical & arithmetic. This output is fed to the set of rotate mux-es on the LOW input and the rotate value $\{a_0 \text{ for 1 level rotate, } a_1, a_0 \text{ for 2, } a_3, a_2, a_1, a_0 \text{ for 4 level}\}$ on the HIGH input. The rotate logic is same as the barrel shifters. Just an extra shift operation is multiplexed at each rotator.

\nearrow Rotate shift

$$\text{Total MUX} = n \log_2 n \text{ (All layers)} + (n-1) + 1 = n(1 + \log_2 n)$$